

**LAGOS CITY POLYTECHNIC, IKEJA**  
**SCHOOL OF ENGINEERING AND APPLIED SCIENCE**  
**DEPARTMENT OF ELECTRICAL AND ELECTRONICS ENGINEERING**  
**2015/2016 SEMESTER EXAMINATION**

<b>COURSE</b>	<b>TITLE:</b>	<b>ELECT.</b>	<b>MEASUREMENT</b>
<b>COURSE CODE:</b>	<b>&amp; INSTRUMENTATION II</b>	<b>NO</b>	<b>OF QUESTIONS : 6</b>
<b>FOR WHOM:</b>	<b>EEC 235/236</b>	<b>TIME</b>	<b>ALLOWED: 2 HRS</b>
<b>ANSWER</b>	<b>ND YR III</b>	<b>CE, EE</b>	<b>INSTRUCTIONS:</b>
		<b>PT</b>	
		<b>ANY</b>	

**FOUR QUESTIONS**

1. A coil consists of a resistance of  $100\Omega$  and an inductance of  $200\text{mh}$ . If an alternating voltage,  $V$  given by  $V = 200 \sin 500t$  volts is applied across the coil, Calculate.
  - (a) the circuit impedance
  - (b) the current flowing
  - (c) the potential difference across the resistance
  - (d) the potential difference across the inductances
  - (e) the phase angle between voltage and current
  
2. (a) Draw and explain the operation of a power factor meter.  
 (b) A dynamometer type wattmeter with its voltage coil connected across the load side of the instruments read  $250\text{w}$  if the load voltage is  $200\text{v}$ , what power is being taken by load? The voltage coil branch has a resistance of  $2000\Omega$ .
  
3. Two wattmeter indicates  $10\text{kw}$  and  $3\text{kw}$  respectively when connected to measure the input power to a 3-phase balanced load the reverse switch being operated on the meter indicated  $3\text{kw}$  reading. Determine  
 (a) the input power (b) the load power factor.
  
4. (a) Draw the block diagram of cathode Ray oscilloscope  
 (c) A cathode Ray Oscilloscope has a time base and signal amplitude control switch being set at  $100\mu\text{s}/\text{cm}$  and  $20\text{v}/\text{cm}$  respectively to produce a square wave form having a width of one complete cycle as  $5.2\text{cm}$  on the screen. If the peak height of the wave form is  $3.6\text{cm}$  then Calculate the  
 (i) Periodic time (ii) frequency  
 (iii) peak to peak voltage (iv) Amplitude
  
5. (a) List and explain six factors of the instrument selection in three(3) major classes of instrument.  
 (b) Explain the importance of Humidity measurement II find the power factor of a motor, when its output power is  $3024\text{w}$  and the current is  $18\text{A}$  from the source voltage of  $240\text{v}$ .
  
6. (a) List and explain 6 factors of the instrument selection in three major classes of instrument.  
 (b) Explain the importance of humidity measurement in an industry.