

**LAGOS CITY POLYTECHNIC, IKEJA**  
**SCHOOL OF ENGINEERING & APPLIED SCIENCE**  
**DEPARTMENT OF ELECTRICAL/ELECTRONICS ENGINEERING**  
**2015/2016 SEMESTER EXAMINATION**

<b>COURSE</b>	<b>TITLE:</b>	<b>ELECTRICAL</b>	<b>CIRCUIT</b>
	<b>THEORY 1</b>		
<b>COURSE CODE:</b>	<b>EEC 239/EEC 232</b>	<b>NO OF QUESTION :</b>	<b>6</b>
<b>FOR WHOM:</b>	<b>ND YR II EE/CE</b>	<b>TIME ALLOWED:</b>	<b>2 HRS</b>
<b>ATTEMPT</b>	<b>ANY</b>	<b>PT</b>	<b>INSTRUCTIONS:</b>

**4 QUESTIONS**

1. (a) State the Trigonometric form and polar form of representing AC signals respectively.  
 (b) Express  $5\angle 53.1^\circ$  in j-notation form.  
 (c) If  $V_1 = 10 + j20$  and  $V_2 = 20 + j30$ , find the sum of  $V_1$  and  $V_2$ , express the result in polar form.  
 (d) Given the following two vectors  $A = 20\angle 60^\circ$  and  $B = 5\angle 30^\circ$  perform the following indicated operation (i)  $A \times B$  (ii)  $A/B$
2. (a) Explain why it is most convenient to multiply or divide by first of all converting to polar form?  
 (b) With the aid of a waveform, differentiate between purely inductive circuit and purely capacitive circuit.  
 (c) Draw the phasor diagram for Inductive circuit and capacitive circuit  
 (d) When is an A. C circuit said to be in Resonance?
3. (a) A resistance of  $10\Omega$  is connected in series with pure inductance of  $100\text{MH}$  and the circuit is connected across a  $100\text{v}$ ,  $50\text{HZ}$  supply. Calculate  
 (i) the circuit current (ii) the voltage across each element  
 (iii) the power factor of the circuit  
 (iv) the power consumed.  
 (b) Draw the phasor diagram for R-L-C series A.C circuit
4. (a) A circuit having a resistance of  $1256$ , an inductance of  $0.15\text{H}$  and a capacitance of  $100\mu\text{F}$  in series, is connected across a  $100\text{v}$ ,  $50\text{HZ}$  supply. Calculate  
 (a) the impedance (b) the current  
 (c) the voltage across R, L and C (d) The power factor of the circuit.
5. (a) A circuit consists of a  $115\Omega$  resistor in parallel with a  $41.5\mu\text{F}$  capacitor and is connected to a  $230\text{v}$ ,  $50\text{HZ}$  supply. Calculate  
 (i) The branch currents (ii) The power factor (iii) The power consumed  
 (b) Give the 5 conditions for series resonance of A.C circuit.
6. (a) The bandwidth of a series resonance circuit is  $130\text{HZ}$  and the resonance frequency is  $1300\text{HZ}$ , find the Q-factor of the circuit.  
 (b) State Thevenins Theorem (c) State Nortons Theorem  
 (d) Apply Thevenins Theorem to find the current through the Resistance R as Shown in